

ASSIGNMENT- 2 AND 3

HARDWARE DESIGN METHODOLOGY

RUCHI MEC2021005
NAVYA MEC2021020
TEJAS MEC2021015

MTECH 2ND SEM



Question

This assignment needs to be performed using LT-SPICE. Please adhere to the deadlines strictly.

Note:

* For SPICE simulation kindly use 180 nm technology library by PTM. Details of the model file can be found here: http://ptm.asu.edu/modelcard/180nm_bulk.txt

*For SPICE-based assignment, use output load capacitance to be **500 fF** in your design (if not stated).

Take $V_{DD} = 1.8$ V.

* It is necessary to show the calculations/ steps done to design the circuit.

* Schematic needs to be neat and clean. It should be labeled properly.

* Copying the report/ plagiarism shall result in 0 marks

* All the necessary simulation snapshots need to be included with white background. Labels should be visible

* A group size of a maximum of 3 students is permissible


Statement 1.

(8+2 marks)

Implement TSPC positive edge-triggered D Flip Flop (Follow the Textbook for the design).

Compute its setup and hold time. Optimize its power delay product. Compute the maximum operating frequency.

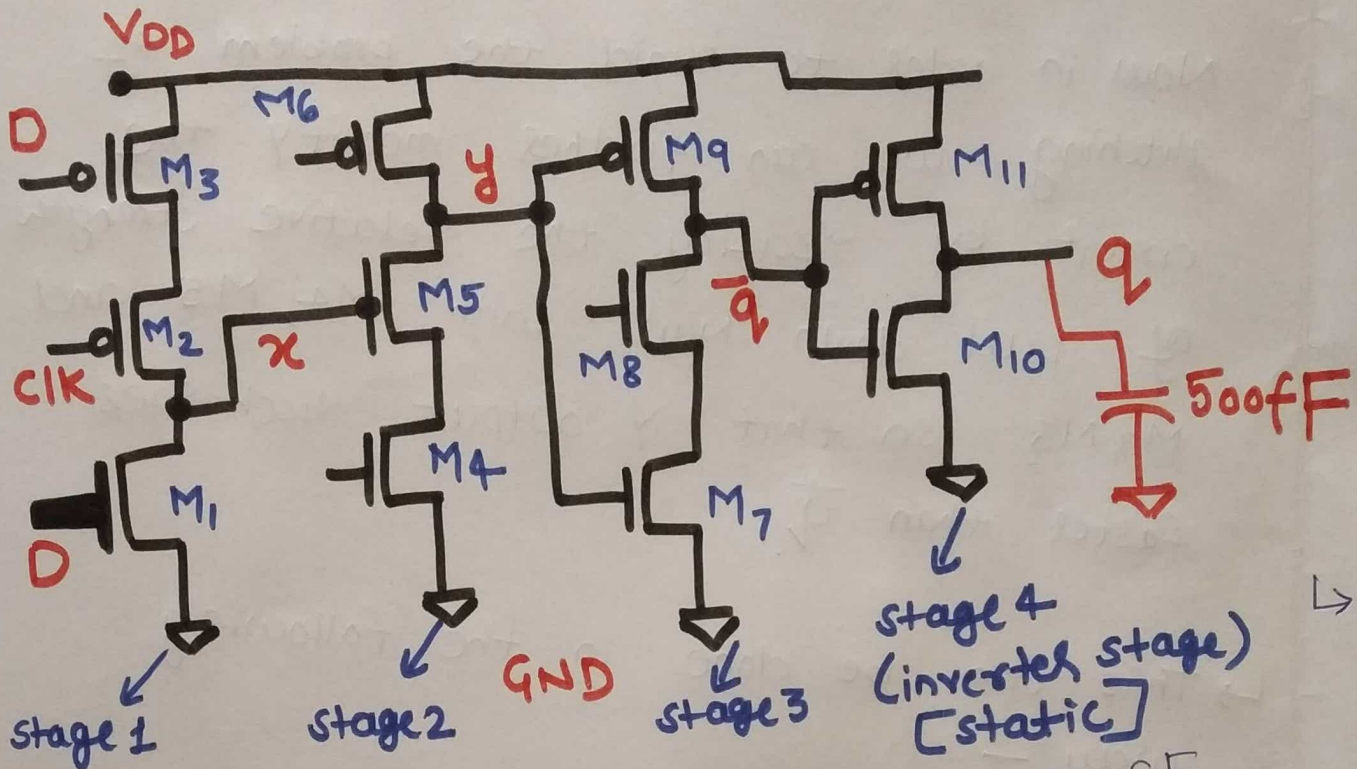⇒ For optimizing the circuit completely let us calculate and apply modified values of (W/L) for each of the Tx.



As we have been given a $C_{load} = 500fF$
 let us optimize the given circuit to have
 stage ratio of 2 with $l_n/l_p = 4/1$

(using 180nm mode file)

Part ① → optimization for (W/L)

⇒ stage 4 -

$$\frac{C_L}{C_4} = 2 = \frac{500}{C_4}$$

$$\Rightarrow C_4 = 250fF$$

$$\text{but } C_4 = C_{gate} = WL C_{ox}$$

$$\text{where } L = 180nm$$

$$C_{ox} = \frac{\epsilon_{SiO_2}}{C_{ox}}$$

$$\therefore L C_{ox} = 180 \times 10^{-9} \times \frac{8.85 \times 3.97 \times 10^{-12}}{4 \times 10^{-9}}$$

$$\therefore LC_{Op} = 1581.052 \times 10^{-12}$$

$$\Rightarrow \omega_T LC_{Op} = 250 \times 10^{-15}$$

$$\text{but } \therefore \omega_n / \omega_p = 4/1$$

$$\therefore \omega_p = 4 \times \omega_n$$

$$\therefore \omega_T = \omega_n + \omega_p = \omega_n + 4\omega_n = 5\omega_n$$

$$\therefore 5\omega_n \times 1581.052 \times 10^{-12} = 250 \times 10^{-15}$$

$$\therefore \boxed{\omega_n = 31.6 \text{ rad/s}} \quad (M_{10})$$

$$\text{and } \omega_p = 4 \times 31.6 \text{ rad/s}$$

$$\therefore \boxed{\omega_p = 126.4 \text{ rad/s}} \quad (M_{11})$$

→ Stage 3 -

$$\frac{C_4}{C_3} = 2 \Rightarrow C_3 = \frac{C_4}{2} = \frac{250}{2} = 125 \text{ fF}$$

$$\therefore \boxed{C_3 = 125 \text{ fF}}$$

$$\Rightarrow 5\omega_n LC_{Op} = 125 \times 10^{-15}$$

$$5 \times \omega_n \times 1581.052 \times 10^{-12} = 125 \times 10^{-15}$$

$$\therefore \boxed{\omega_n = 15.81 \text{ rad/s}} \quad (M_7, M_8)$$

$$\text{and } \omega_p = 4 \times 15.81 \text{ rad/s}$$

$$\therefore \boxed{\omega_p = 63.24 \text{ rad/s}} \quad (M_9)$$

→ stage 2 - $\frac{C_3}{C_2} = 2 \Rightarrow \frac{125}{2} = C_2$

$\therefore C_2 = 62.5 \text{ fF}$

$\Rightarrow 5\omega_n \times 1581.052 \times 10^{-12} = 62.5 \times 10^{-15}$

$\therefore \omega_n = 7.9 \text{ } \mu\text{m}$ (M4, M5)

and $\omega_p = 4 \times 7.9 \text{ } \mu\text{m}$

$\therefore \omega_p = 31.6 \text{ } \mu\text{m}$ (M6)

→ stage 1 -

$\frac{C_2}{C_1} = 2 \Rightarrow C_1 = \frac{C_2}{2} = \frac{62.5}{2}$

$\therefore C_1 = 31.25 \text{ fF}$

$\Rightarrow 5\omega_n \times 1581.052 \times 10^{-12} = 31.25 \times 10^{-15}$


$5\omega_n \times 1581.052 \times 10^{-12} = 31.25 \times 10^{-15}$

$\therefore \omega_n = 3.95 \text{ } \mu\text{m}$ (M1)

and $\omega_p = 4 \times 3.95 \text{ } \mu\text{m}$

$\therefore \omega_p = 15.8 \text{ } \mu\text{m}$ (M2, M3)

Optimized Circuit

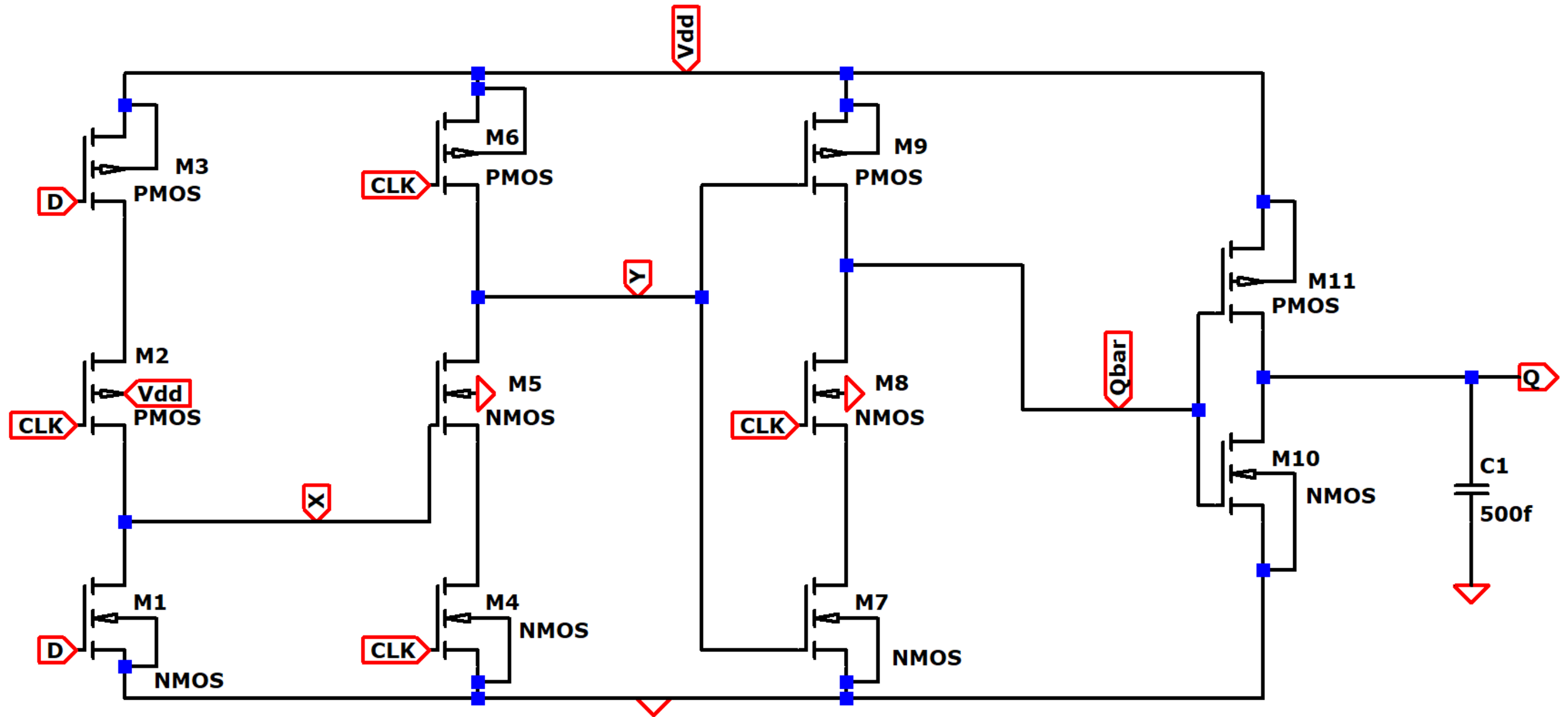

Optimized circuit Netlist

```
M9 Vdd Y Qbar Vdd PMOS l=180nm w=63.24u
M8 Qbar CLK 3 0 NMOS l=180nm w=7.905u
M7 3 Y 0 0 NMOS l=180nm w=7.905u
M6 Vdd CLK Y Vdd PMOS l=180nm w=31.6u
M5 Y X 2 0 NMOS l=180nm w=15.8u
M4 2 CLK 0 0 NMOS l=180nm w=15.8u
M11 Vdd Qbar Q Vdd PMOS l=180nm w=126.5u
M10 Q Qbar 0 0 NMOS l=180nm w=31.625u
M3 Vdd D 1 Vdd PMOS l=180nm w=15.8u
M2 1 CLK X Vdd PMOS l=180nm w=15.8u
M1 X D 0 0 NMOS l=180nm w=3.95u
V1 Vdd 0 1.8
V2 CLK 0 PULSE(0 1.8 0 0.01n 0.01n 7n 14n)
V3 D 0 PULSE(0 1.8 7.077n 0.01n 0.01n 7n 14n)
C1 Q 0 500f
.model NMOS NMOS
.model PMOS PMOS
|
* PSPICE TSMC180nm.lib file RWN 04/18/2010
* library file for transistor parameters for TSMC 0.18 micron process
* uses BIM parameters added 01/15/98
* can configure and attach to Nbreak and Pbreak transistors in PSpice
****
***** 180nm TSMC parameters *****
*T14B SPICE BSIM3 VERSION 3.1 PARAMETERS
* downloaded from MOSIS 04/18/10
*http://www.mosis.com/cgi-bin/cgiwrap/umosis/swp/params/
* tsmc-018/t92y_mm_non_epi_thk_mtl_params.txt
*SPICE 3f5 Level 8, Star-HSPICE Level 49, UTMOST Level 8
* DATE: Jun 8/01
* LOT: T14B WAF: 06
* Temperature_parameters=Default
*$
.MODEL TSMC180nmN NMOS ( LEVEL = 7
+VERSION = 3.1 TNOM = 27 TOX = 4.1E-9
+XJ = 1E-7 NCH = 2.3549E17 VTH0 = 0.354505
+K1 = 0.5733393 K2 = 3.177172E-3 K3 = 27.3563303
+K3B = -10 W0 = 2.341477E-5 NLX = 1.906617E-7
+DVT0W = 0 DVT1W = 0 DVT2W = 0
+DVT0 = 1.6751718 DVT1 = 0.4282625 DVT2 = 0.036004
+U0 = 327.3736992 UA = -4.52726E-11 UB = 4.46532E-19
```

↳ Part ② - optimization for glitches


Now in order to avoid the problem of glitching we can further modify the circuit by resizing the relative strength of pull down n/w with M_4, M_5 and M_7, M_8 so that y output discharges faster than \bar{q} .

↳ This can be done in the following way -


$$M_4, M_5 = 2 \times (w/L)_{4,5} = 15.8 \mu m$$

$$M_7, M_8 = \frac{1}{2} \times (w/L)_{7,8} = \frac{15.8}{2} \mu m \\ = 7.905 \mu m$$

optimization for glitches

 

Before

 

After

optimized Output



→ calculations for STA -

The input must be kept stable before and after the rising edge of the CLK.

From simulation and the type of model file (180 umc T14B BSIM3 version 3.1 Tsmc)


we got 1 inverter delay found to be 77.639 ps.

As the hold time and setup time both should retain their values for 1 inv delay,


$$\therefore t_h = t_s = 77.639 \text{ ps}$$

and also the tc-q delay comes out to be 3×77.639 (excluding the static 4th stage inv) is = 232.917 ps

inverter delay and clock to q

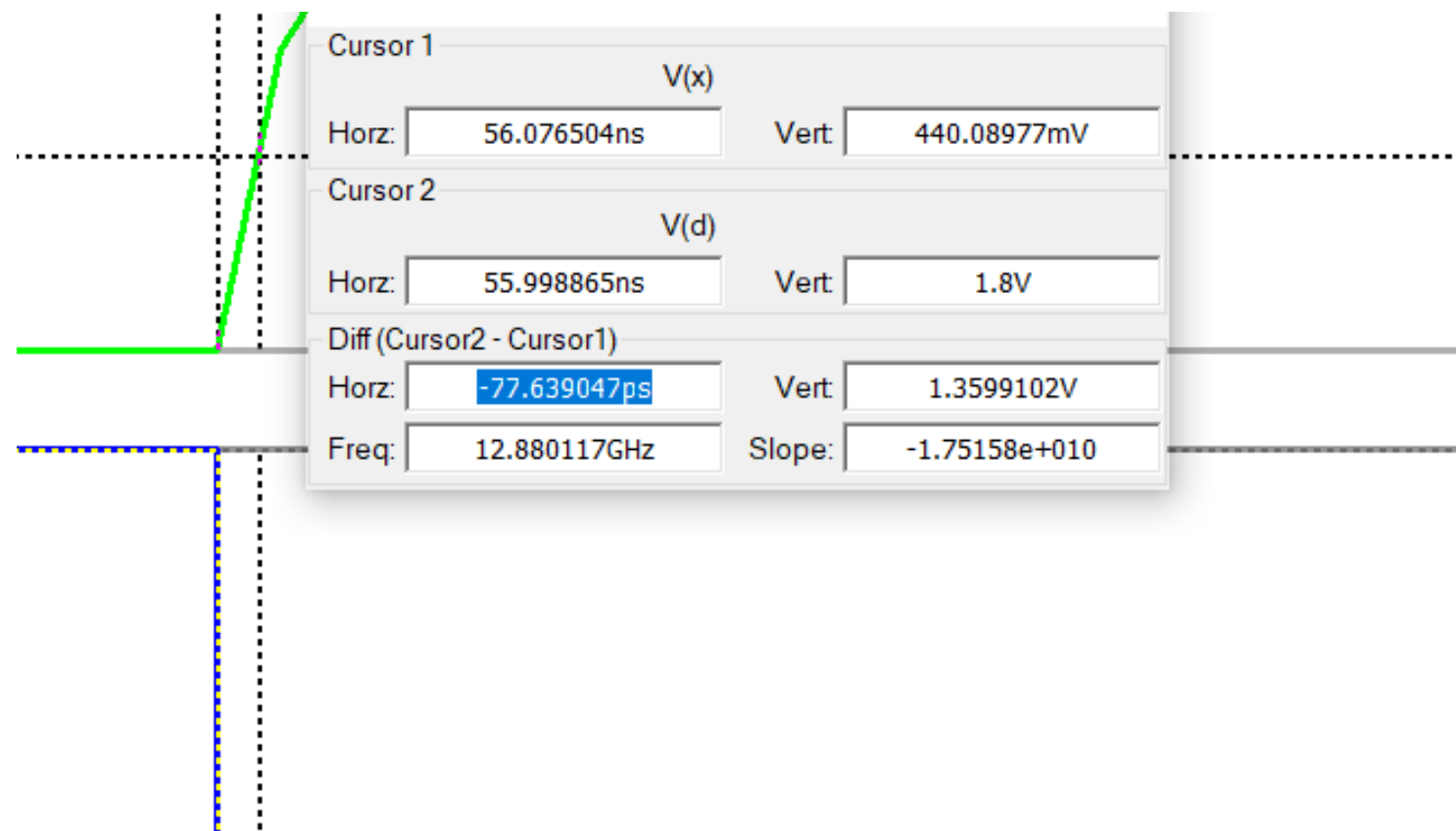

one inverter delay

 

clock to q delay

↳ The operating (max^m) frequency can be calculated as -

$$T \geq t_{c-q} + t_{logic} + t_s$$

$$T \geq (3 \times 77.639) + 77.639 + 77.639$$

$$T \geq 388.195 \text{ ps}$$

$$\text{hence, } f_{max} = \frac{1}{T} = \frac{1}{388.195}$$

$$\Rightarrow \boxed{f_{max} = 2.576 \text{ GHz}}$$

↳ Calculation for power delay product -

PDP is the average energy consumed per switching event.

And its value can be calculated as

$$PDP = P_{avg} \times T_p = [C_L \times V_{DD}^2] / 2$$

(and its unit is $\text{watts} \cdot \text{sec} = \text{Joule}$)

for us, $C_L = 500 \text{ fF}$
and $V_{DD} = 1.8$

$$\therefore PDP = 500 \times 10^{-15} \times (1.8)^2 \times \frac{1}{2}$$

$$\Rightarrow \boxed{PDP = 810 \text{ fJoule}}$$


Question

Statement 2.

(8+2 marks)

Implement a Band Gap reference Circuit, with $V_{ref} = 1.2 \text{ V}$, Temp. coefficient $\leq 200 \text{ ppm/}^{\circ}\text{C}$ (for the worst case). **You can use any topology of your choice.** Also, show V_{out} vs. V_{DD} and minimize the effect of supply voltage variation in output voltage.

→ CTAT calculations —

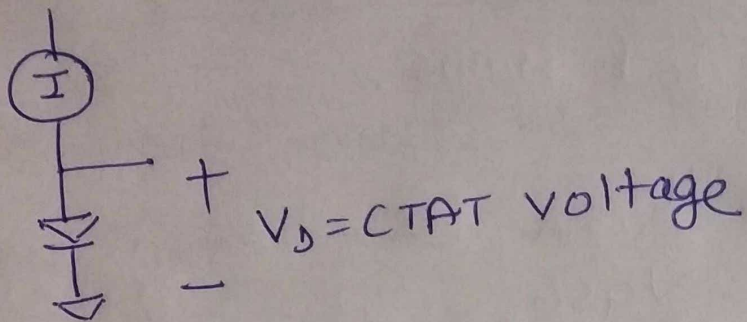


$$\frac{\partial V_D}{\partial T} = V_D - (4+m) V_T - E_g/q$$

for $m = -1.5$
 $V_T = 26 \text{ mV}$
 $T = 300^\circ \text{K}$


we have $\frac{\partial V_D}{\partial T} = -1.88 \text{ mV}/^\circ \text{K}$

and from the simulations done we
got $\frac{\partial V_D}{\partial T} = -1.4 \text{ mV}/^\circ \text{C}$

CTAT

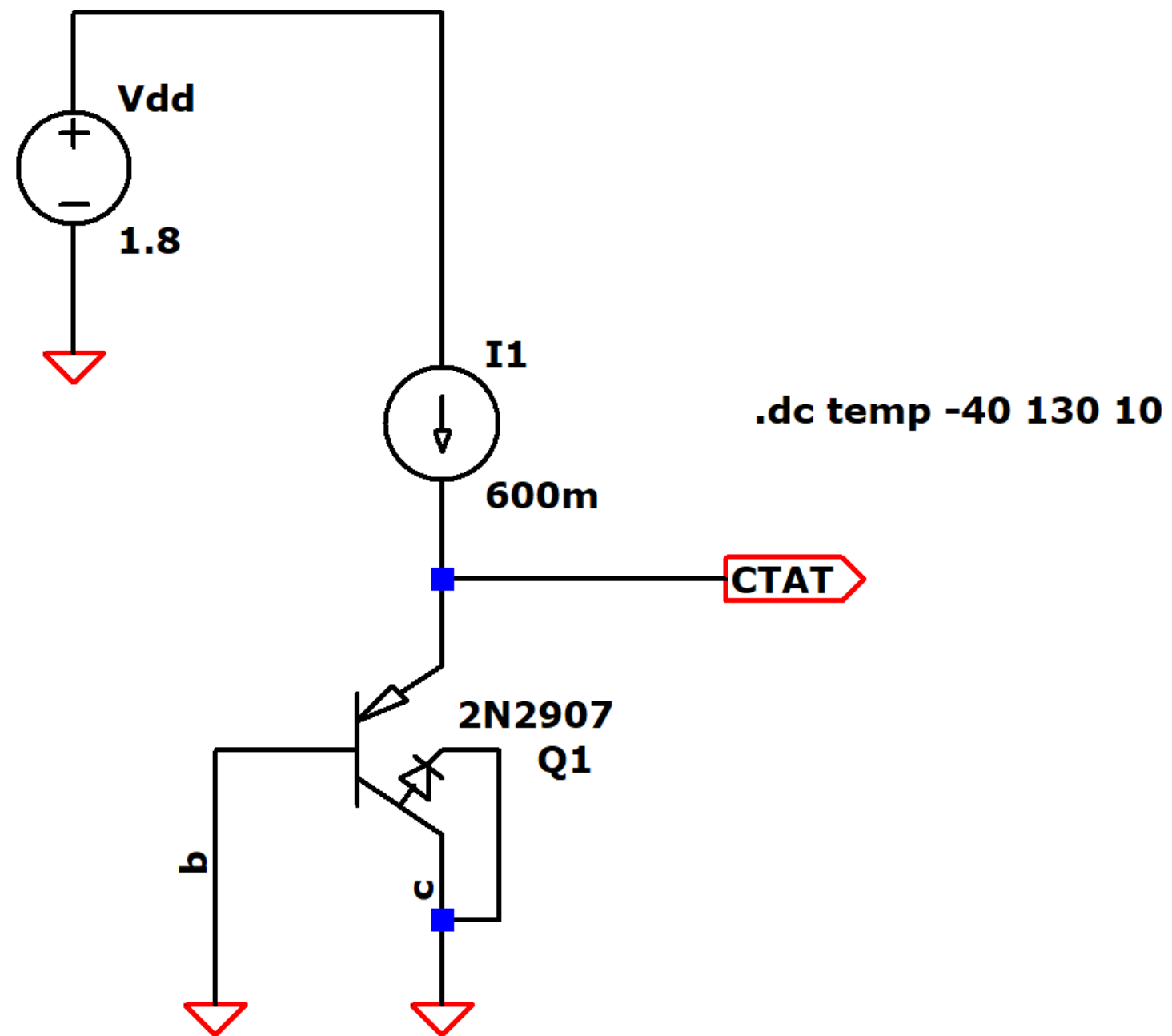


CTAT simulation

 

CTAT simulation

V(ctat)

 

↳ PTAT and BGR calculations -

$$\therefore V_T = \frac{kT}{q} \quad \therefore \boxed{V_T \propto \text{Temp}^\wedge}$$

and also $V_D = V_T \ln \frac{I_0}{I_s} \rightarrow \text{CTAT}$

but $V_{D1} = V_T \ln \frac{I_0}{n I_s} \rightarrow \text{PTAT}$


$$\Rightarrow V_D - V_{D1} = V_T \ln(n)$$

also for our simulations;


$$V_{R2} = \frac{R_2}{R_1} V_T \ln(n)$$

$$\begin{aligned} \frac{\partial V_{R2}}{\partial T} &= \frac{\partial V_T}{\partial T} = \frac{k}{q} = \frac{1.38 \times 10^{-23}}{1.6 \times 10^{-19}} \\ &= 87 \mu\text{V}/^\circ\text{K} \end{aligned}$$

PTAT

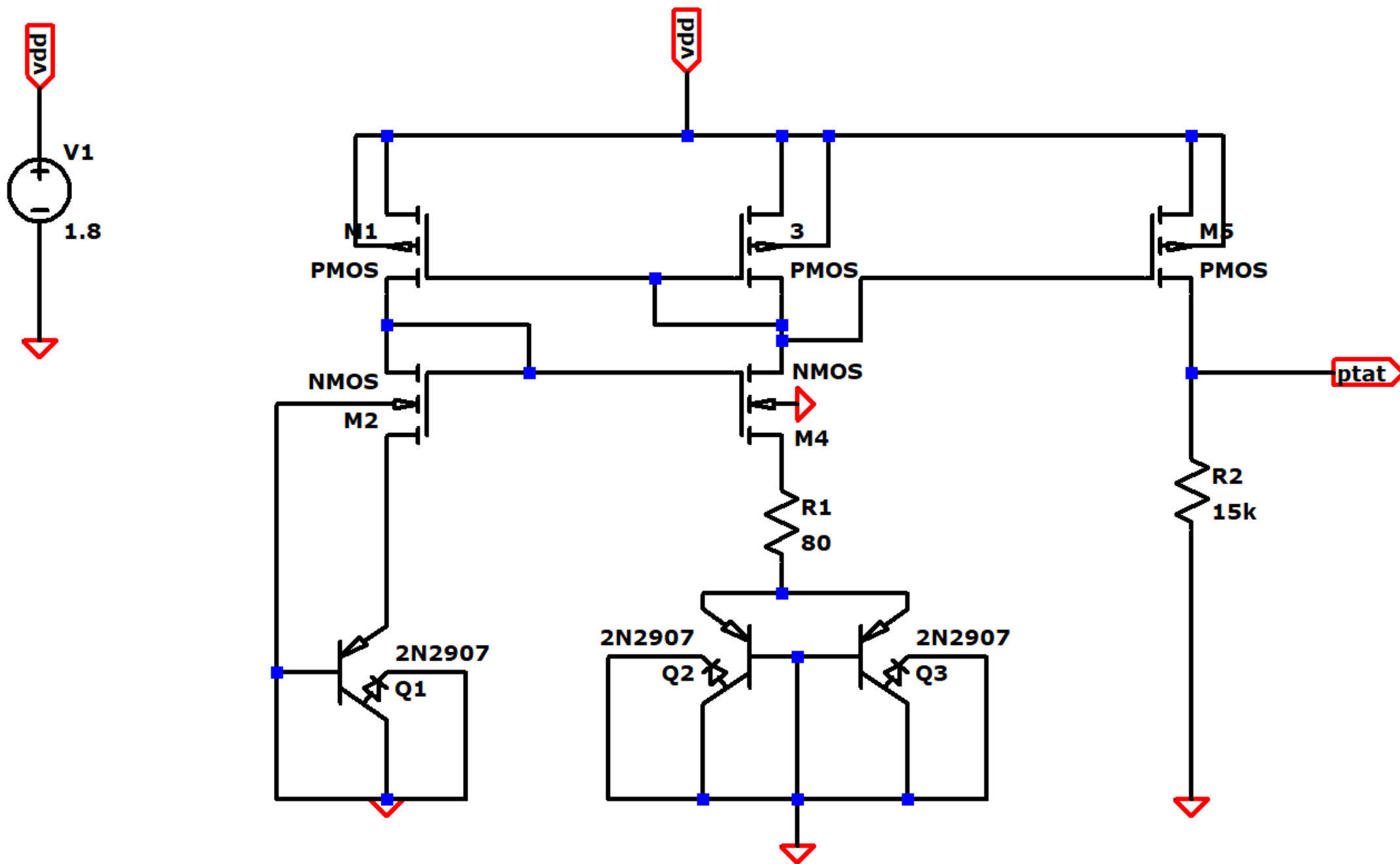

PTAT simulation

 

↳ Note - To improve our BGR responses we increase our (W/L) ratios for pmos and nmos.

The other reason for this is to make it as much as independent of the tempⁿ variations

$$\Rightarrow V_{REF} = V_{EB3} + \frac{R_2}{R_1} \times V_T \times \ln(n)$$

$$1.2 = 0.7 + \frac{R_2}{R_1} \times 0.026 \ln(n)$$

$$\Rightarrow \boxed{19.23 = \frac{R_2}{R_1} \ln(n)}$$

for ideal cases we have

$$\frac{\partial V_{REF}}{\partial T} = \frac{\partial V_T}{\partial T} \times \frac{R_2}{R_1} \ln(n) + \frac{\partial V_{EB3}}{\partial T} = 0$$


↳ for making it zero tempⁿ coeff.

also for the ideal cases we have—


$$\frac{R_2}{R_1} \ln(n) \times 0.087 \text{ mV}/^\circ\text{C} - 1.5 \text{ mV}/^\circ\text{C} = 0$$

$$\Rightarrow \boxed{\frac{R_2}{R_1} \ln(n) = 17.2413}$$

BGR circuit

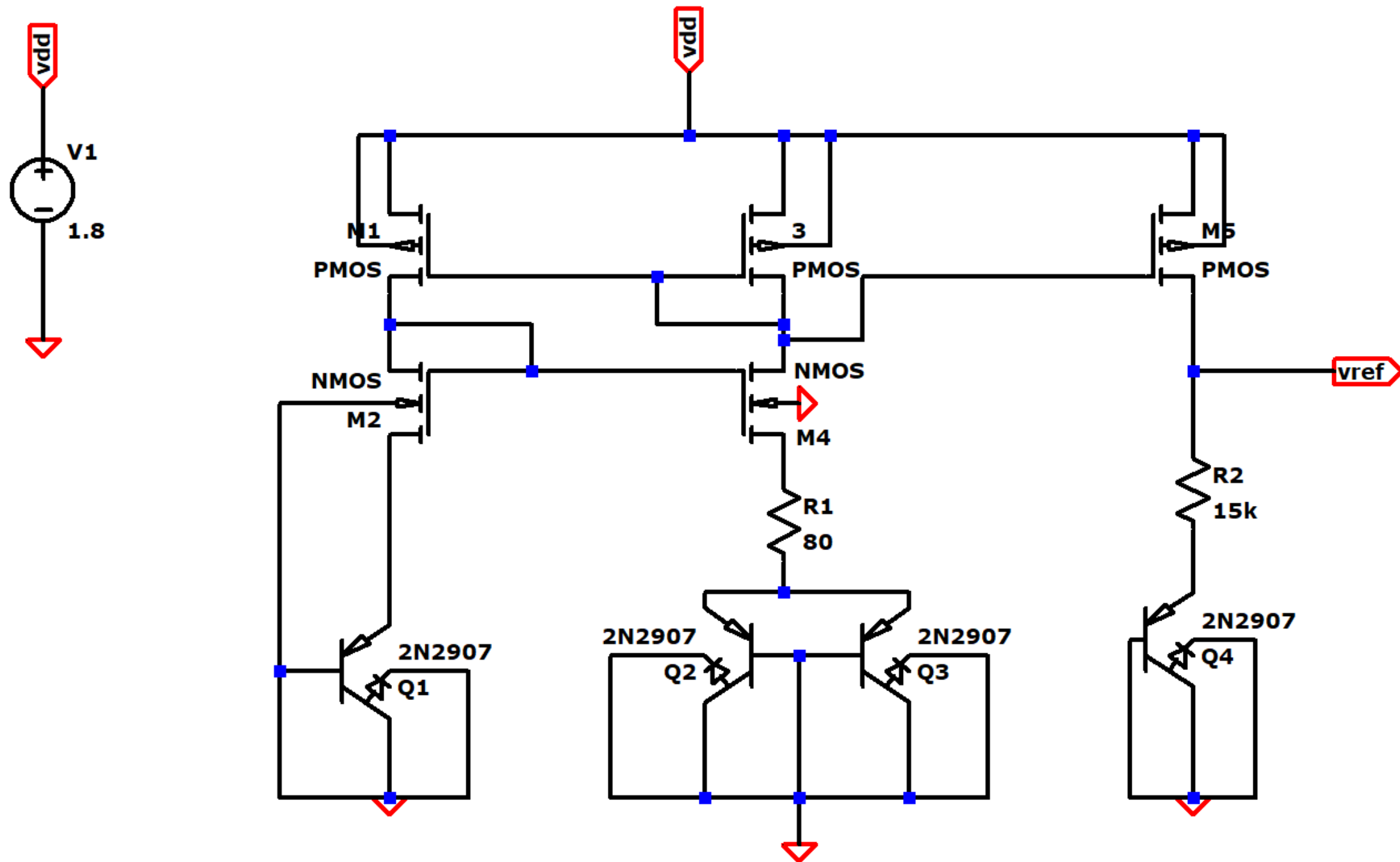


BGR simulation

 

BGR simulation

V(vref)

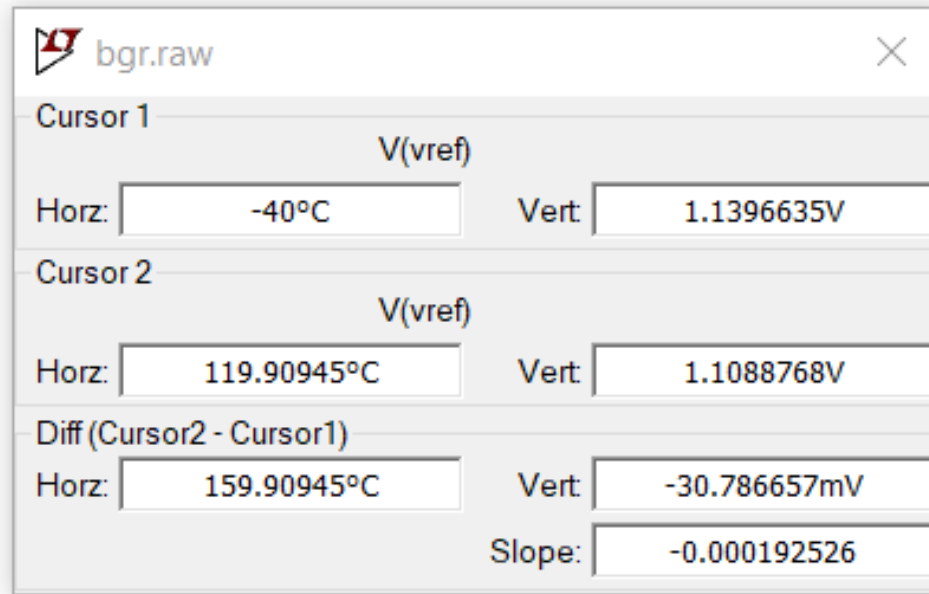

↳ Temp[^] Coeff calculation -


$$\Rightarrow TC = \frac{1}{V_{REF}} \times \frac{\partial V_{REF}}{\partial T}$$

$$= \frac{1}{1.2} \times \frac{30.78 \text{ m}}{120 - (-40)}$$

$$= 160.03125 \text{ ppm}/^{\circ}\text{C} \leq 200 \text{ ppm}/^{\circ}\text{C}$$

effect of increasing supply voltage on vref

V(vref)

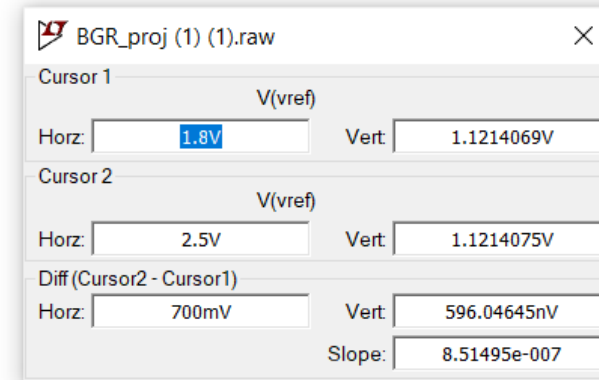

You have reached
end of this document

Thank you